LAB 3 FUNCTIONAL BLOCK DIAGRAM [6:0] Seg OF_S 7-509 [3:0] A. OF. U DisPLAY Complement [3:0]\$ [3:0]B ADDER