

## ECE 2029

### Homework 5 – Solution

C18

#### Problem 1 - 5 points total

- a) Whenever MENU button is pressed, input is given to the system. However, next setting depends on given input as well as the current setting. In other words, the next output state depends on input and current state of the system. Thus, TV remote's menu access system employs **sequential** logic.
- b) Alarm sound is the output of the system. System enable/arming switch is an input to the system and motion sensors can be considered as states of the system. Alarm is sounded only if system is enabled, i.e., output depends only on current input. Thus, home security system employs **combinational** logic.

#### Problem 2)

*Vahid 3.1:* Compute clock period for the following frequencies.

Period = 1/Frequency

- a) 50kHz = 50,000Hz  
Period = 1/50,000Hz = 0.00002s = **20μs**
- b) 300MHz = 300,000,000Hz  
Period = 1/300,000,000Hz = **3.33ns**
- c) 3.4 GHz = 3,400,000,000Hz  
Period = 1/3,400,000,000Hz = **0.294ns**
- d) 10 GHz = 10,000,000,000Hz  
Period = 1/10,000,000,000Hz = **0.100ns**
- e) 1THz = 1,000,000,000,000Hz  
Period = 1/ 1,000,000,000,000Hz = **1.00ps**

*Vahid 3.3:* Compute the clock frequency for the following clock periods

Frequency = 1/Period

a) 1s

$$\text{Frequency} = 1/1 = \mathbf{1\text{Hz}}$$

b) 1ms = 0.001s

$$\text{Frequency} = 1/0.001\text{s} = 1000\text{Hz} = \mathbf{1\text{kHz}}$$

c) 20ns = 0.000000020s

$$\text{Frequency} = 1/0.000000020\text{s} = 50,000,000 = \mathbf{50\text{MHz}}$$

d) 1ns = 0.000000001s

$$\text{Frequency} = 1/0.000000001\text{s} = 1,000,000,000 = \mathbf{1\text{GHz}}$$

e) 1.5ps = 0.0000000000015s

$$\text{Frequency} = 1/0.0000000000015\text{s} = 1,500,000,000,000 = \mathbf{1.5\text{THz}}$$

**\*\*You can also do these calculations mentally using the prefixes. For example, the prefix “pico” in scientific notation is  $10^{-12}$ . Because the frequency is the inverse of the period (and vice versa), the sign of the exponent is flipped. The prefix “tera” in scientific notation is  $10^{12}$ , so a period of 1.5 picoseconds yields a frequency of 1.5 terahertz.\*\***

### Problem 3)

a) S-R Latch

S	R	Q	Qn
0	0	Last Q	Last Qn
0	1	0	1
1	0	1	0
1	1	0	0


### S-R Latch with Enable (C)

<b>C</b>	<b>S</b>	<b>R</b>	<b>Q</b>	<b>Qn</b>
0	*	*	Last Q	Last Qn
1	0	0	Last Q	Last Qn
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0


### D-Latch with Enable (C)

<b>C</b>	<b>D</b>	<b>Q</b>	<b>Qn</b>
0	*	Last Q	Last Qn
1	0	0	1
1	1	1	0


#### b) S-R Latch

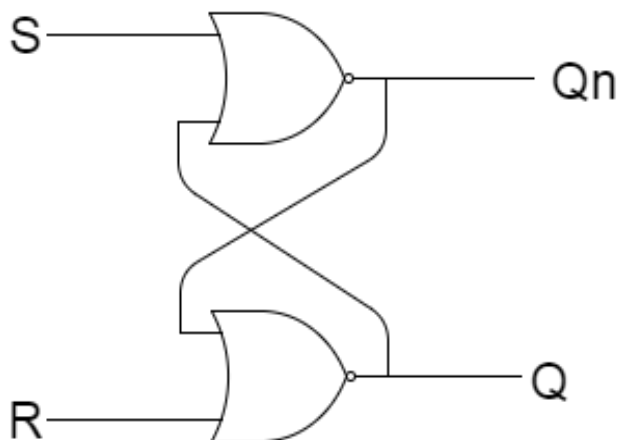

S-R Latch with Enable (C)

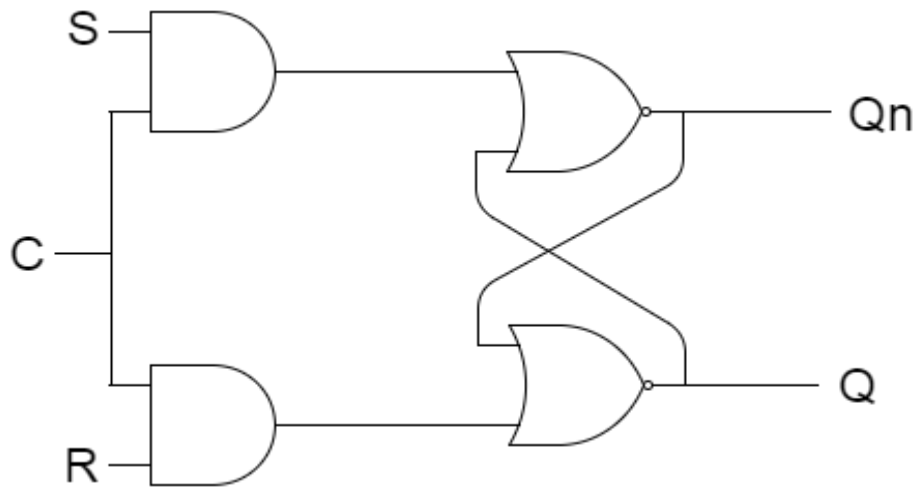


D Latch with Enable

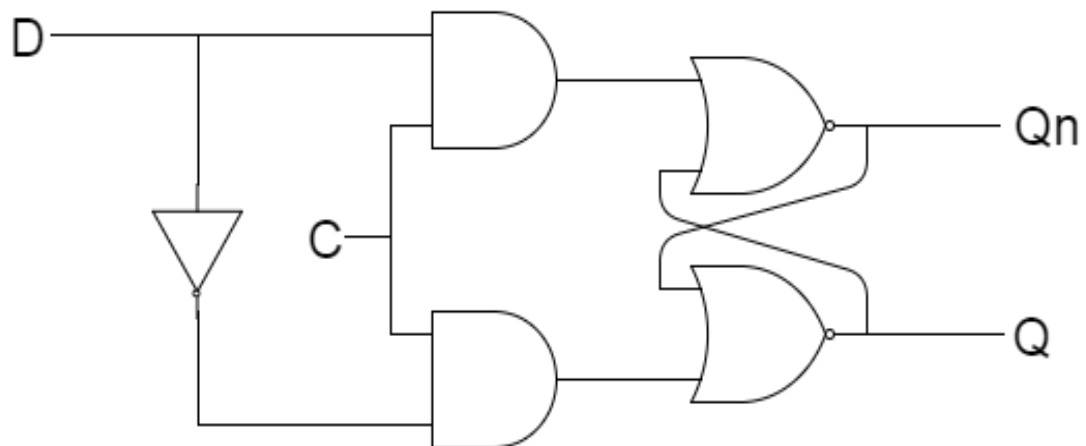

## Problem 4)

Vahid 3.7

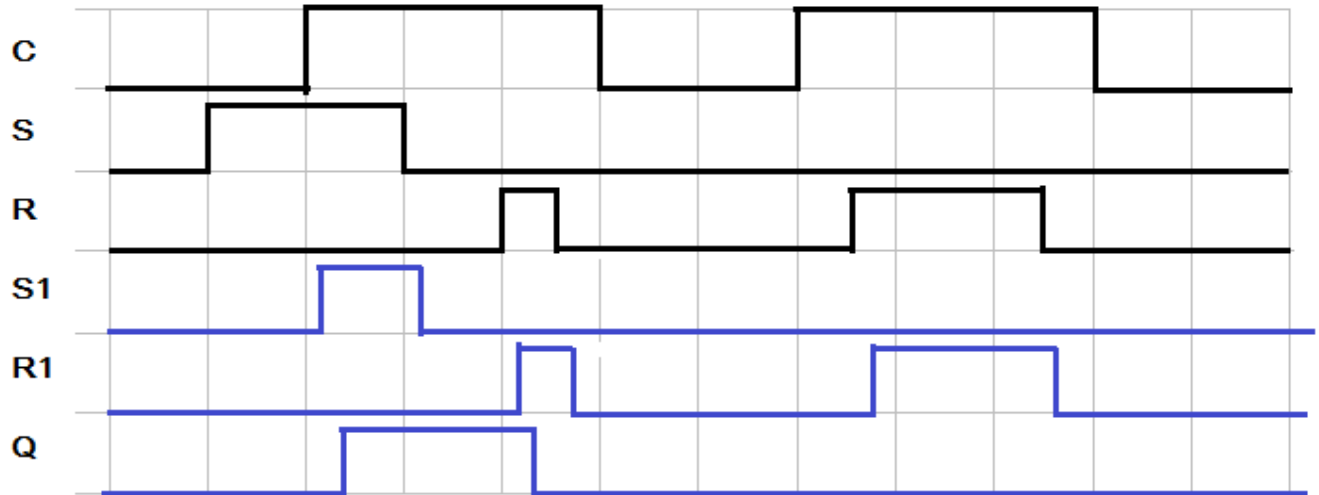

when  $C = 0$

$Q = \text{last } Q$

when  $C = 1$

$Q = 1$  when  $S = 1$  and  $R = 0$

$Q = 0$  when  $S = 0$  and  $R = 1$  or when  $S = 1$  and  $R = 1$



$S1$  follows  $S$ ,  $R1$  follows  $R$

$Q$  does not transition until after  $S1$  and  $R1$  transition

C	S	R	S1	R1	Q	QN
0	*	*	0	0	Last	Last
1	0	0	0	0	Last	Last
1	0	1	0	1	0	1
1	1	0	1	0	1	0
1	1	1	1	1	0	0
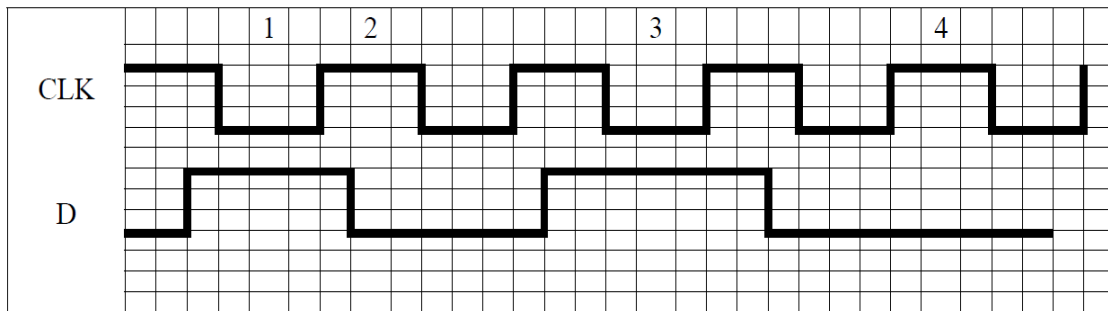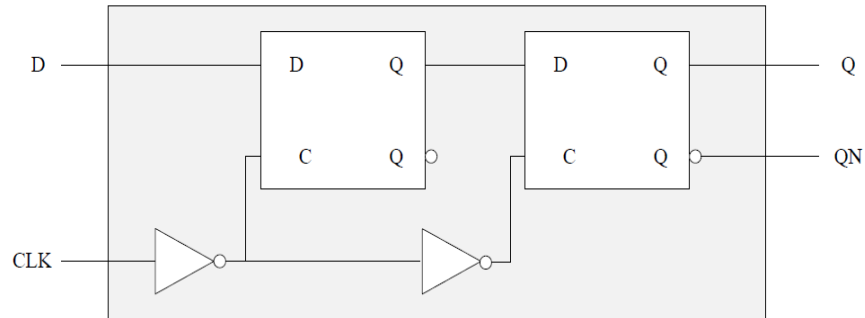
## Problem 5 - 10 points total


The sequential logic component shown below is a positive edge triggered D flip-flop, and contains two D-latches. The timing diagram shows a series of events on the positive-edge triggered flip-flop. Fill in the logic values for Q and QN for the times specified on the diagram with numbered bubbles. The initial value of Q is 0, and QN is 1. (Ignoring the propagation delay)



	Q	QN
Time 1	0	1
Time 2	1	0
Time 3	0	1
Time 4	0	1

## Problem 6 - 20 points total

1) Using D-Latch

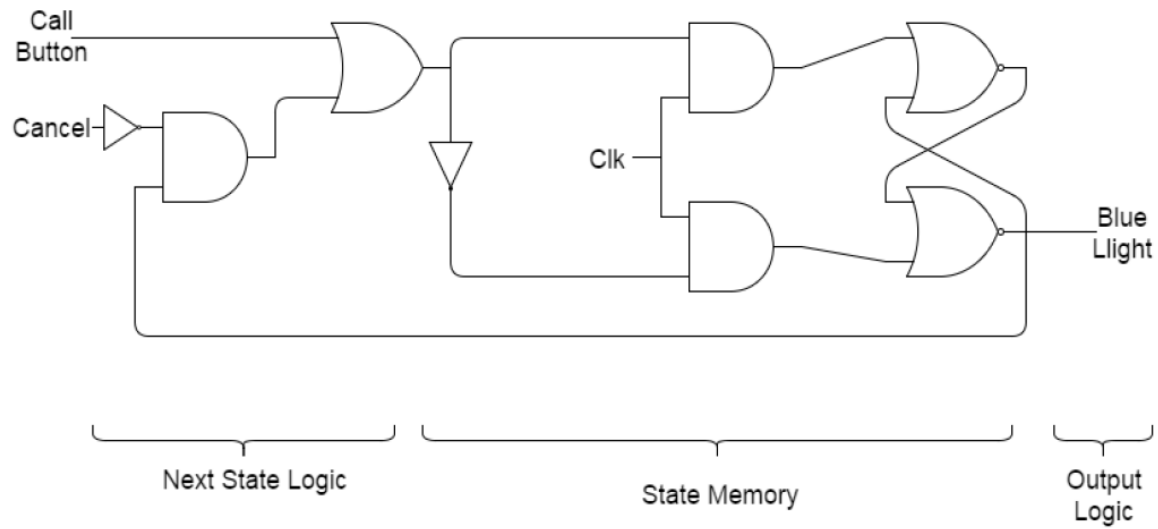

2) Next State Logic:

$$D = \text{Call} + \text{Cancel}'Q$$

$$Q^* = C_0 + C_1'Q$$

(Where  $Q^* = D$ ,  $C_0 = \text{Call}$ , and  $C_1 = \text{Cancel}$ )

Output:

$$Y = Q$$

3)


Call	Cancel	Q	D
0	0	0	0
0	1	0	0
1	0	1	1
1	1	0 1	1

No Change, Memory

Set

Reset

4)

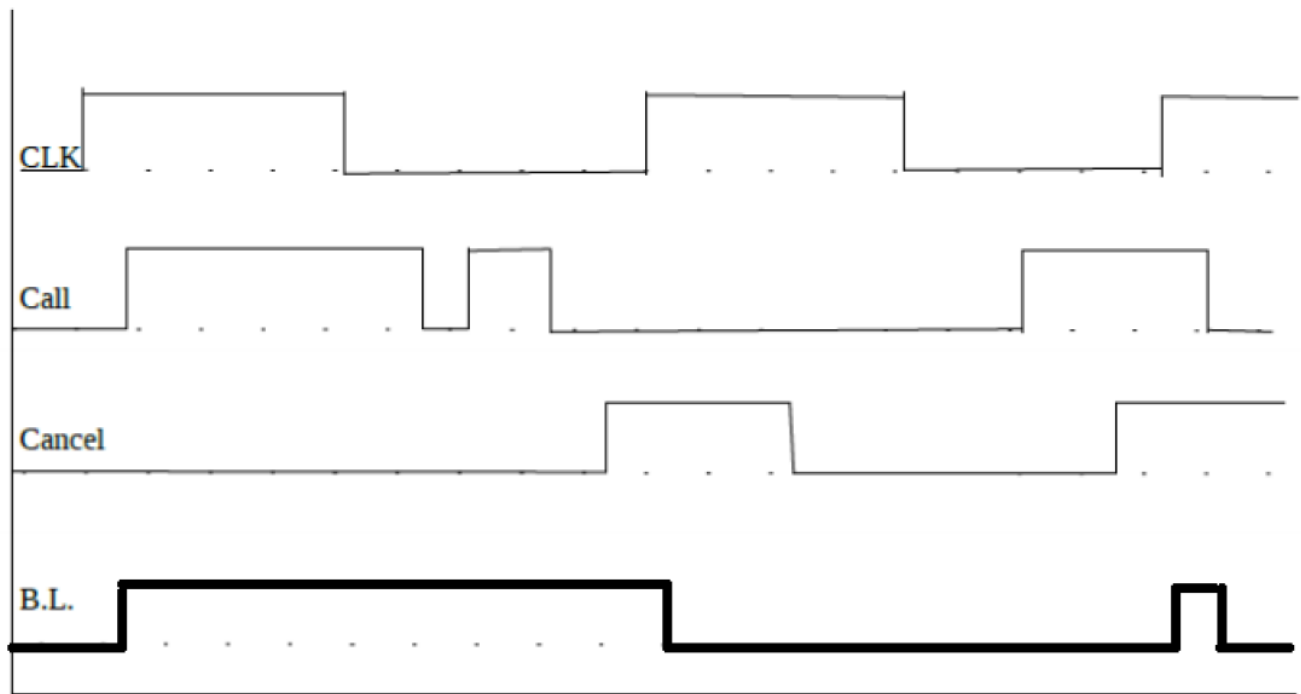

**Problem 7 – 10 points**

