 


**Problem 1 – 40 points total**

For the sequential machine shown:



- a) Determine the Boolean expressions for next state logic and output logic from the circuit. That is, express  $Q_1^*$ ,  $Q_0^*$ , and  $F$  as logic expressions in terms of  $Q_1$ ,  $Q_0$ , and  $X$ .  
(Do not write  $Q_1^*$ ,  $Q_0^*$  logic expressions in terms of  $F$  since  $F$  is the output)

(15 pts)

$$F = X \cdot Q_1 \cdot Q_0$$

$$Q_1^* = \overline{X} \cdot (Q_0 \oplus Q_1)$$

$$Q_0^* = (Q_1 \cdot \overline{Q_0}) + X$$


b) Fill in the state table, given below:

(15 pts)

Present State $Q_0 Q_1$	Input $X$	Next State $Q_0^+ Q_1^+$	Output $F$
0 0	0	0 0	0
0 0	1	1 0	0
0 1	0	0 1	0
0 1	1	1 0	0
1 0	0	1 1	0
1 0	1	1 0	0
1 1	0	0 0	0
1 1	1	1 1	1


c) Draw a state transition diagram for this sequential machine.

(10 pts)

 




 **OPTION 2:** Design a controller for a vending machine. It sells soda only and each cost 75 cents. The machine accepts quarter coins only and one quarter at a time. Once it receives 75 cents, it automatically dispenses a soda can and back to the initial reset state. You do not need to consider the changes or coin return scenarios.



a) Draw a state transition diagram for this vending machine controller.

(5 pts)

 

b) List a state transition table with input, output, current states, and next states.

(10 pts)

Present State	Input	Next State	Output
$Q_1 \quad Q_0$	$X$	$Q_1^+ \quad Q_0^+$	$Y$
0 0	0	0 0	0
0 0	1	0 1	0
0 1	0	0 1	0
0 1	1	1 0	0
1 0	0	1 0	0
1 0	1	0 0	1
1 1	0	X X	X
1 1	1	X X	X

c) Derive the logic expression for the input of each D-Flip Flop and output Y. (15 pts)

$Q_1, Q_0$	00	01	10	11
$Q_1^+$	0	0	X	1
$Q_0^+$	0	1	X	0

$Q_1, Q_0$	00	01	10	11
$Q_1^+$	0	1	X	0
$Q_0^+$	1	0	X	0


$$Q_0^+ = \bar{x}Q_0 + xQ_1$$

$$Q_1^+ = x\bar{Q}_0\bar{Q}_1 + \bar{x}Q_1$$

$$Y = xQ_0$$

$Q_1, Q_0$	00	01	10	11
$Y$	0	0	X	0
$Q_1^+$	0	0	X	1



d) Draw the circuit diagram for the implementation of this circuit. (10 pts)

 



**Problem 3– 20 points total**

  - a) Given the circuit diagram below, complete the waveform for L and F. Assume the D-Flip Flops are rising-edge triggered and initialized to 0. (15 pts)



- b) FPGA implements combinational logic using look-up tables (LUTs). Assume the size of each LUT is only 16-bit that is equivalent to a memory space with 4-bit input and 1-bit output. Fill the LUT contents to implement logic function: (Hint: Use logic cells in K-Map to derive output) (5 pts)

$$Y = B'D' + A'BD + CD' + AD'$$

AB \ CD	00	01	11	10
00	1	0	0	1
01	0	1	1	1
11	1	0	0	1
10	1	0	0	1

Fill the memory contents:

