

Name Solutions

ECE Box _____

ECE 2029

Homework 6

D16

Each problem is worth the number of points shown.

Show your work in a neat, organized and easily followed sequence if you expect to get any partial credit. This assignment is due **Thursday, April 26** by 5 pm at the ECE office AK202.

Problem 1 -20 points total

The following sequential circuit is a Pulse Distributor:

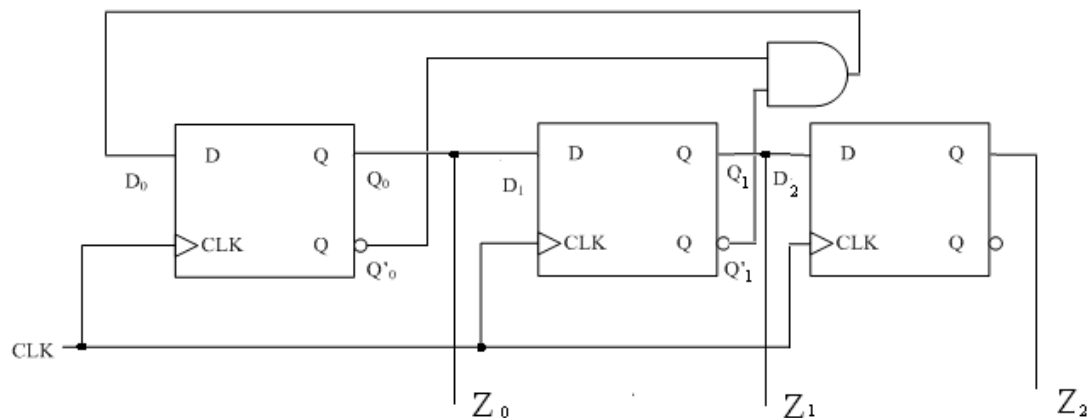


Figure 1

Notice: This sequential circuit does not have the input signal and the output Z is the present state of D flip-flop. The initial condition of output is set as 000.

- a) (5 pts) Determine Boolean expressions for next state logic and output logic from the circuit. That is, express D_2 , D_1 , D_0 and Z_2 , Z_1 , Z_0 as logic expressions in terms of Q_2 , Q_1 and Q_0 . (do **not** write D logic expression in terms of Z since Z is the output)

Output logic expression: $Z_0 = Q_0^n, Z_1 = Q_1^n, Z_2 = Q_2^n$



Next state logic expression: $Q_0^{n+1} = D_0 = \overline{Q_0^n} \overline{Q_1^n}, Q_1^{n+1} = D_1 = Q_0^n,$

$Q_2^{n+1} = D_2 = Q_1^n$

b) (10 pts) Fill in the state table, given below.

Present State(Output)	Next State
$Q_2^n \ Q_1^n \ Q_0^n$	$Q_2^{n+1} \ Q_1^{n+1} \ Q_0^{n+1}$
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	1 0 0
0 1 1	1 1 0
1 0 0	0 0 1
1 0 1	0 1 0
1 1 0	1 0 0
1 1 1	1 1 0

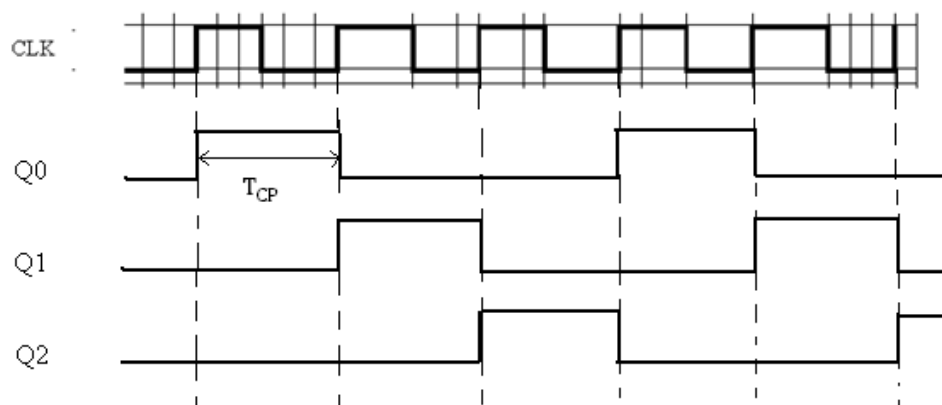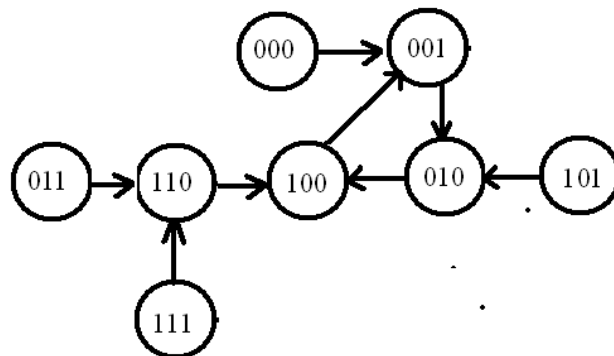
c) (10 pts) Draw a state transition diagram and timing diagram for this sequential machine.



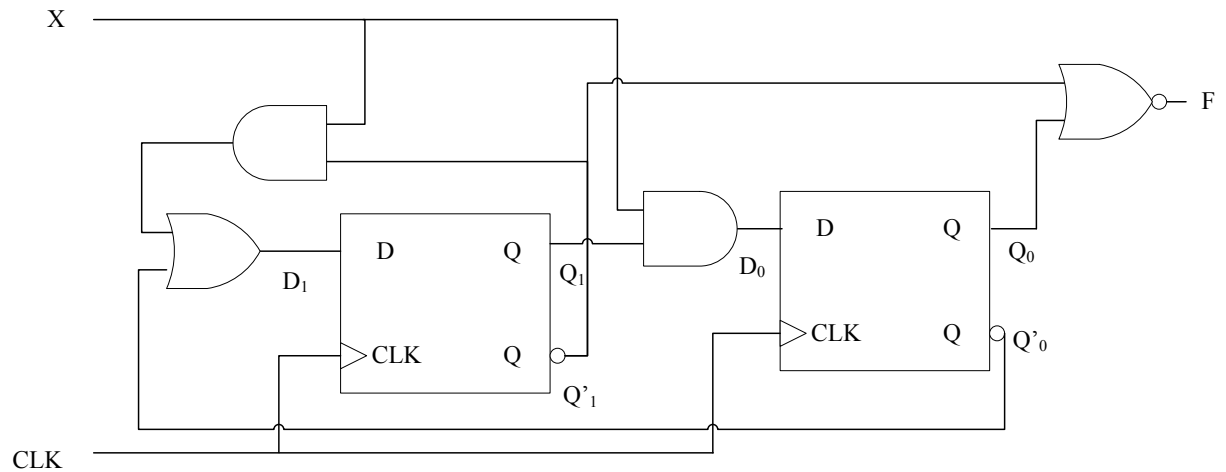d) (5 pts) From the timing diagram, what the logic function of this sequential circuit.
 Answer: We can see from timing diagram, this sequential circuit is a Pulse Distributor.

It assigns a pulse with pulse width T_{CP} (period of CLK) to three outputs sequentially.

For the sequential machine in the circuit diagram:



- a) (15 total, each 5 pts) Determine Boolean expressions for next state logic and output logic from the circuit. That is, express D_1 , D_0 and F as logic expressions in terms of Q_1 , Q_0 and X .

$$D_1 = Q_1'X + Q_0'$$



$$D_0 = Q_1 X$$

$$F = (Q_1' + Q_0)' \text{ or } Q_1 Q_0'$$

- b) (10 pts total, each wrong 1 pt) Fill in the state table, given below.


Present State	Input	Next State	Output
$Q_1 \ Q_0$	X	$D_1 \ D_0$	F
0 0	0	1 0	0
0 0	1	1 0	0
0 1	0	0 0	0
0 1	1	1 0	0
1 0	0	1 0	1
1 0	1	1 1	1
1 1	0	0 0	0
1 1	1	0 1	0

c) (5 pts) Draw a state transition diagram for this sequential machine.

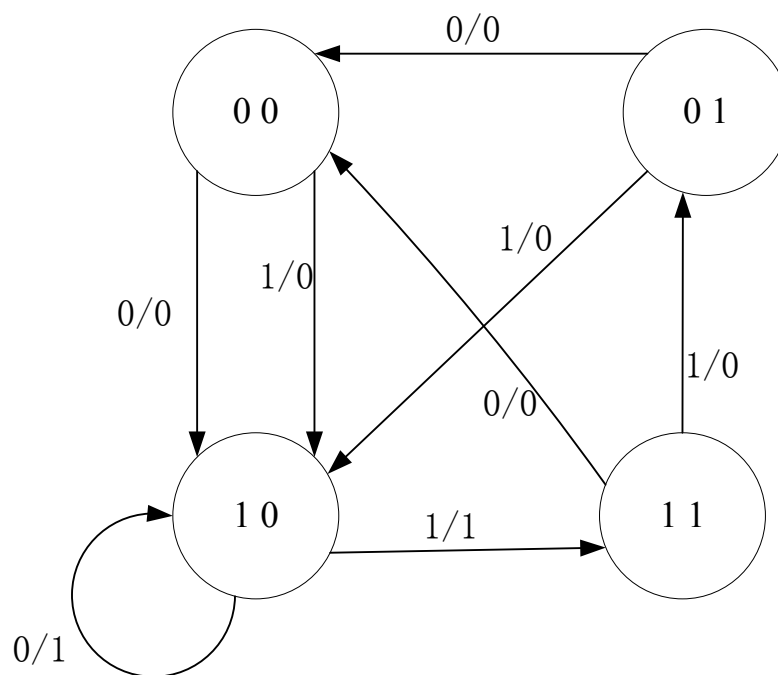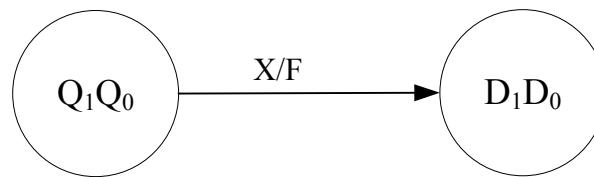

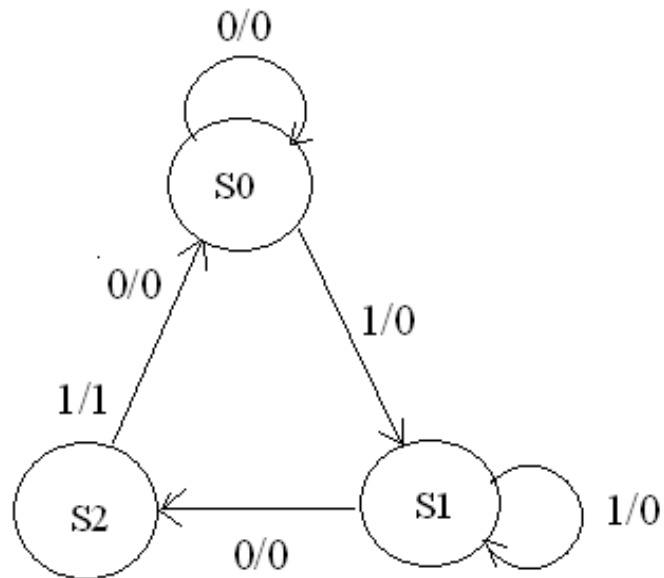Problem 3 - 30 points total

Applying the same procedure as in Problem 2, use positive-edge triggered D flip-flop to design a sequential circuit following the transition diagram shown in figure below.



First, find the state table:

Present State		Input	Next State	Output
Q_1	Q_0	X	Q_1^+ Q_0^+	F
0	0	0	0 0	0
0	0	1	0 1	0
0	1	0	1 0	0
0	1	1	0 1	0
1	0	0	0 0	0
1	0	1	0 0	1
1	1	0	d d	d
1	1	1	d d	d

$\bar{X} \backslash Q_1^n Q_0^n$	00	01	11	10
0	0	1	d	0
1	0	0	d	0

$$Q_1^{n+1} = Q_0^n \bar{X}$$

$\bar{X} \backslash Q_1^n Q_0^n$	00	01	11	10
0	0	0	d	0
1	1	1	d	0

$$Q_0^{n+1} = Q_1^n X$$


$\bar{X} \backslash Q_1^n Q_0^n$	00	01	11	10
0	0	0	d	0
1	0	0	d	1

$$F = Q_1^n X$$

Then, we have the characteristic equation of D flip-flop as: $\mathbf{D = Q^{n+1}}$

Thus, we can get $D_1 = Q_0^n \bar{X}$, $D_0 = \bar{Q}_1^n X$

Now draw the sequential circuit as:

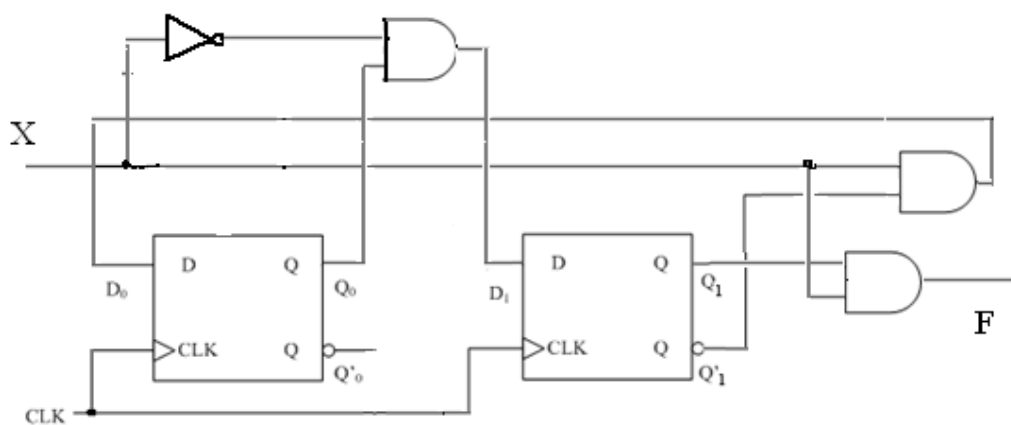


Problem 4 - 30 points total

Let us design a simple vending machine that sells drinks only. Each bottle costs 75 cents. It only accepts dollar bills and quarters. Once it receives 75 cents, a bottle is dispensed. If the current balance is more than 75 cents, it dispenses a drink and also pays the change in quarters. Design a FSM to implement the vending machine. The input signals include dollar bill and quarter insertion. The output signals are drink dispense and the number of quarters as change which could be 0 to 3. Since the circuit clock is very fast, it is safe to assume that quarter and dollar bill are not inserted at the same time.

- Draw the state transition diagram;
- Provide a complete table with input, output, current and next states.
- Apply K-map to obtain the logic expressions.
- Draw the circuit diagram using D flip-flops.


a)

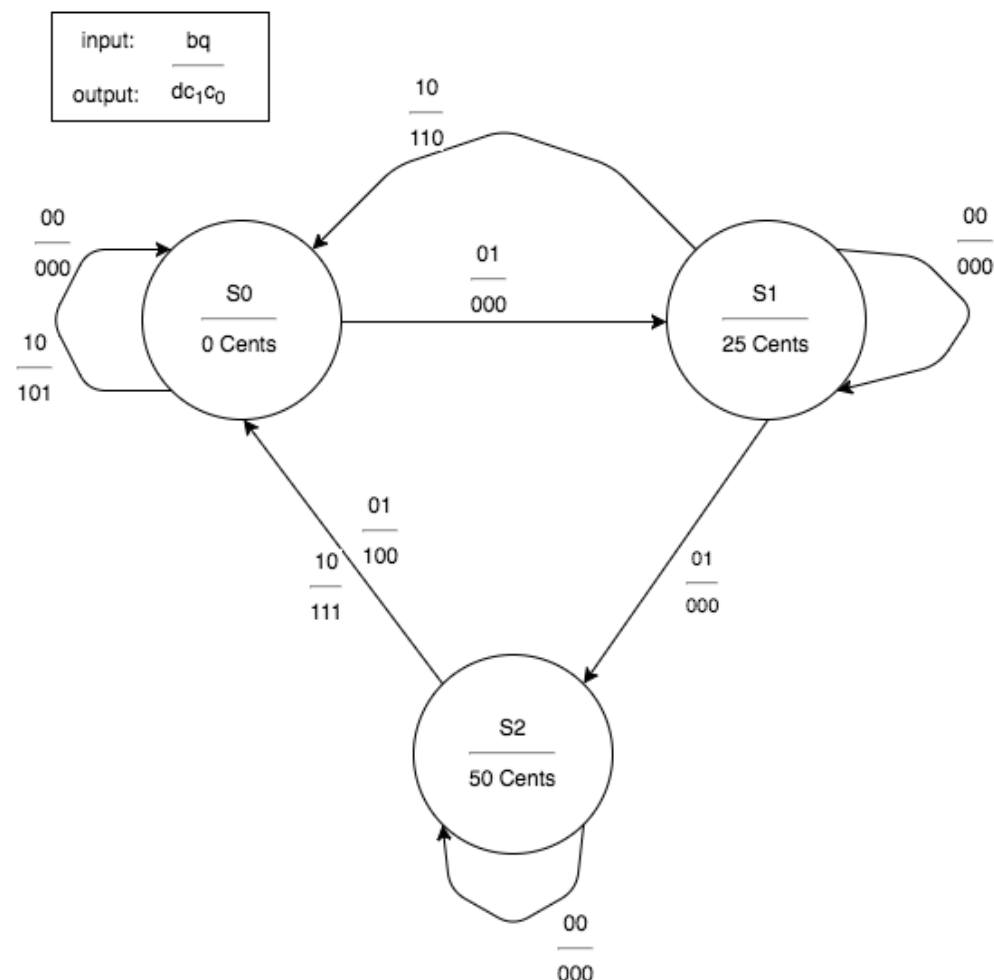

current state

next state

change



bill	quarter	Q1	Q0	Q1+	Q0+	disp	c1	c0
0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0
0	0	1	0	1	0	0	0	0
0	0	1	1	X	X	X	X	X
0	1	0	0	0	1	0	0	0
0	1	0	1	1	0	0	0	0
0	1	1	0	0	0	1	0	0
0	1	1	1	X	X	X	X	X
1	0	0	0	0	0	1	0	1
1	0	0	1	0	0	1	1	0
1	0	1	0	0	0	1	1	1
1	0	1	1	X	X	X	X	X
1	1	0	0	X	X	X	X	X
1	1	0	1	X	X	X	X	X
1	1	1	0	X	X	X	X	X
1	1	1	1	X	X	X	X	X

$$Q_1^+ = \overline{b}qQ_1 + qQ_0$$

Q ₁ Q ₀ \ bq	00	01	11	10
00	0	0	X	1
01	0	1	X	0
11	X	X	X	X
10	0	0	X	0

$$Q_0^+ = q\overline{Q_1}Q_0 + \overline{b}qQ_0$$

Q ₁ Q ₀ \ bq	00	01	11	10
00	0	1	X	0
01	1	0	X	0
11	X	X	X	X
10	0	0	X	0

$$\text{disp} = b + qQ_1$$

Q ₁ Q ₀ \ bq	00	01	11	10
00	0	0	X	0
01	0	0	X	1
11	X	X	X	X
10	1	1	X	1

$$c_1 = qQ_1 + bQ_0 + bQ_1$$

Q ₁ Q ₀ \ bq	00	01	11	10
00	0	0	X	0
01	0	0	X	1
11	X	X	X	X
10	1	1	X	1

$$c_0 = b\overline{Q_0}$$

Q ₁ Q ₀ bq	00	01	11	10
00	0	0	X	0
01	0	0	X	0
11	X	X	X	X
10	1	0	X	1

d)

